
Lecture 10

Multi-Cycle Implementation




Today's Menu

► **Multi-Cycle machines**

- ▷ Why multi-cycle?
- ▷ Comparative performance
- ▷ Physical and Logical Design of Datapath and Control
- ▷ Microprogramming


Multi-cycle Solution

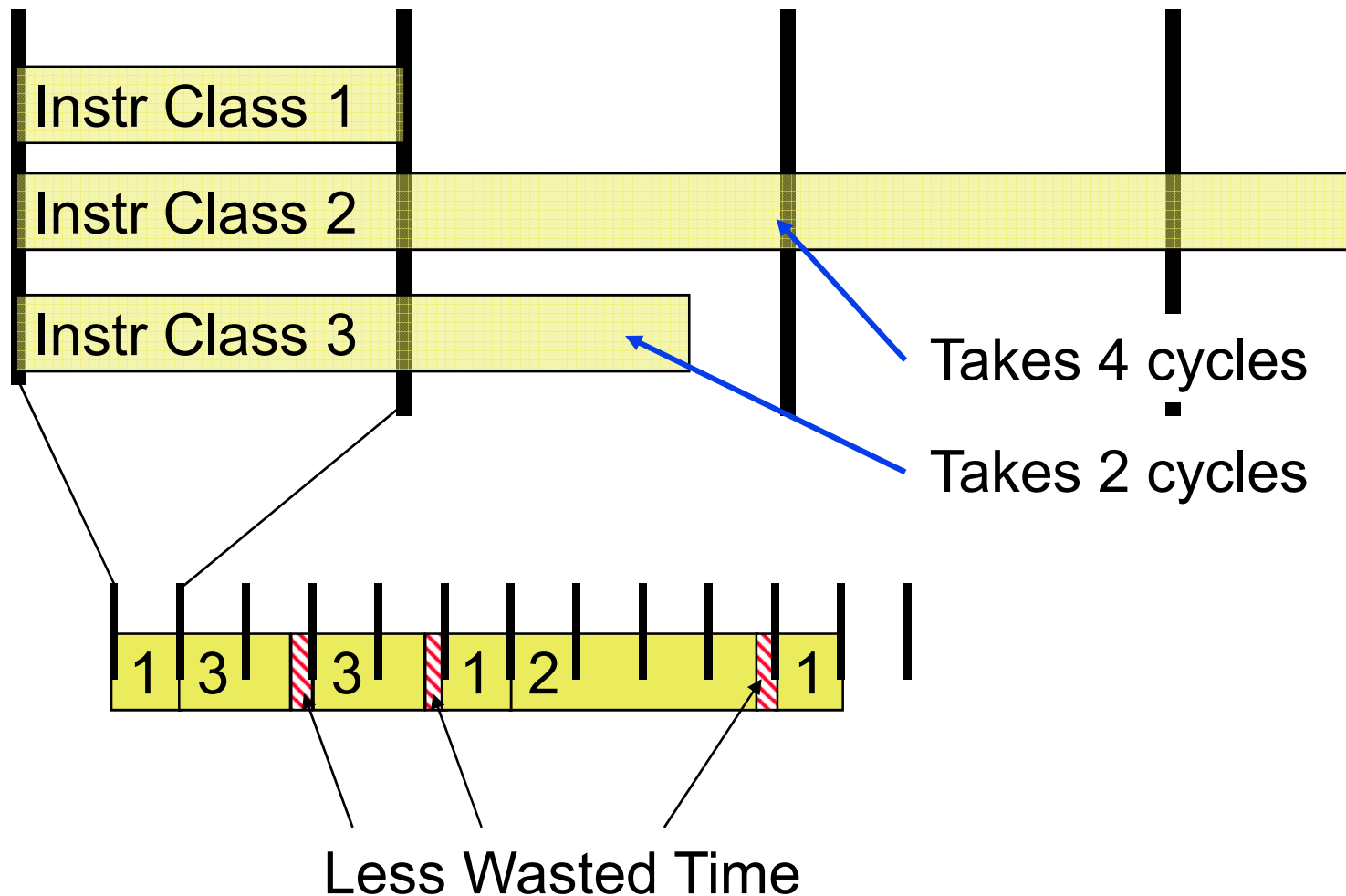Idea: Let the FASTEST instruction determine clock period




Multi-cycle Reality

 - ▶ We are going to go further than allowing the fastest instruction to determine rate
- ▶ We are going to break EVERY instruction up into phases



MIPS Architecture Instruction Classes

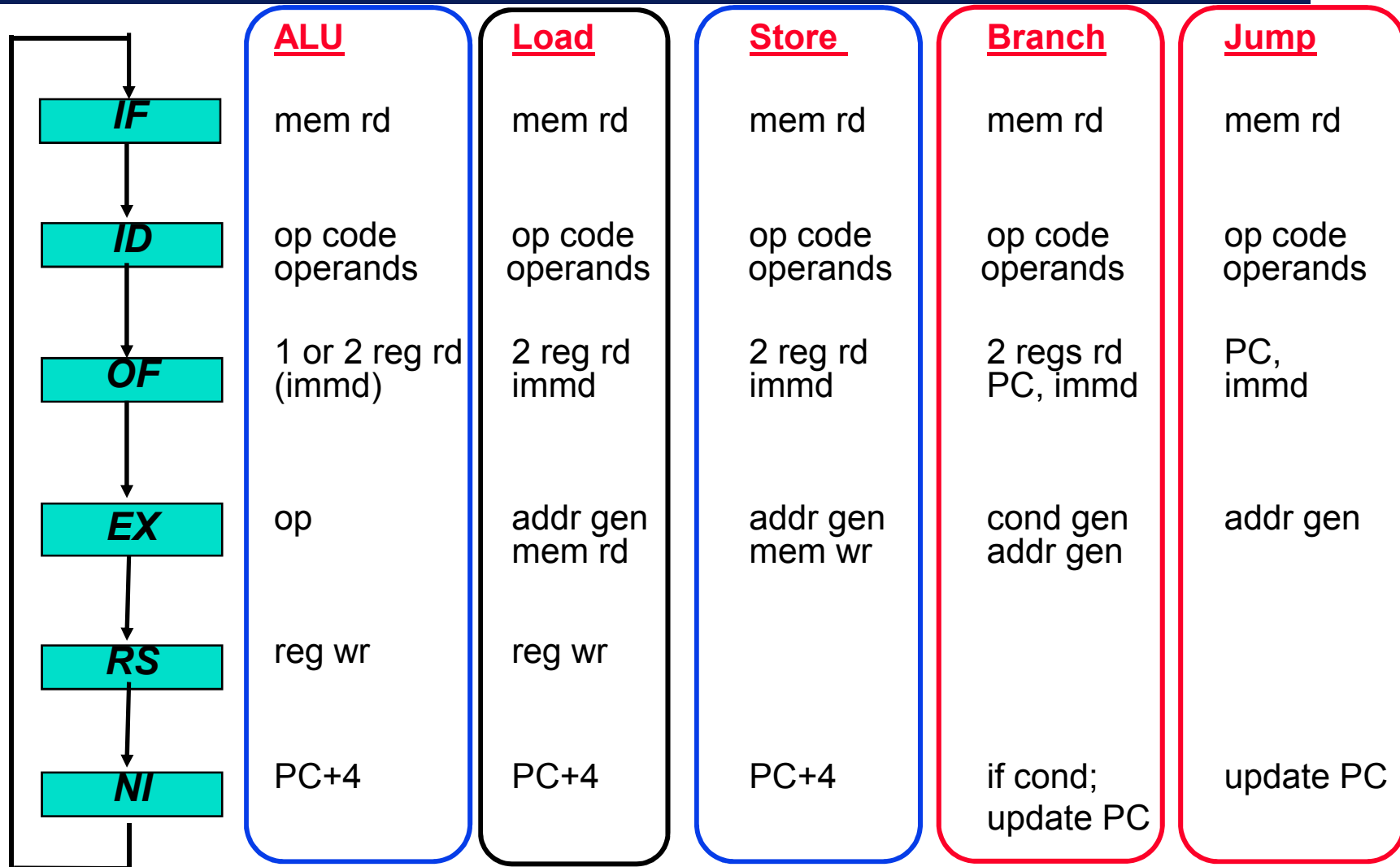


Note That...

- ▶ **Instruction decode and register read must be done for all classes of instructions**
- ▶ **PC+4 can be done right after fetch**
- ▶ **Address generation for Jump can be performed during the decode step**
- ▶ **The same adder can be shared among:**
 - ▷ Instruction fetch logic ($PC = PC + 4$)
 - ▷ Address generation logic ($Address = A + IR[15:0]$)
 - ▷ Branch target calculation ($Next\ PC = (PC + 4) + IR[15:0]$)
 - ▷ ALU operations ($ALUOutput = A + B$)
- ▶ **Same memory port can be used to access instructions and data**

Full Diagram of Multi-cycle Machine

► Figure 5.33

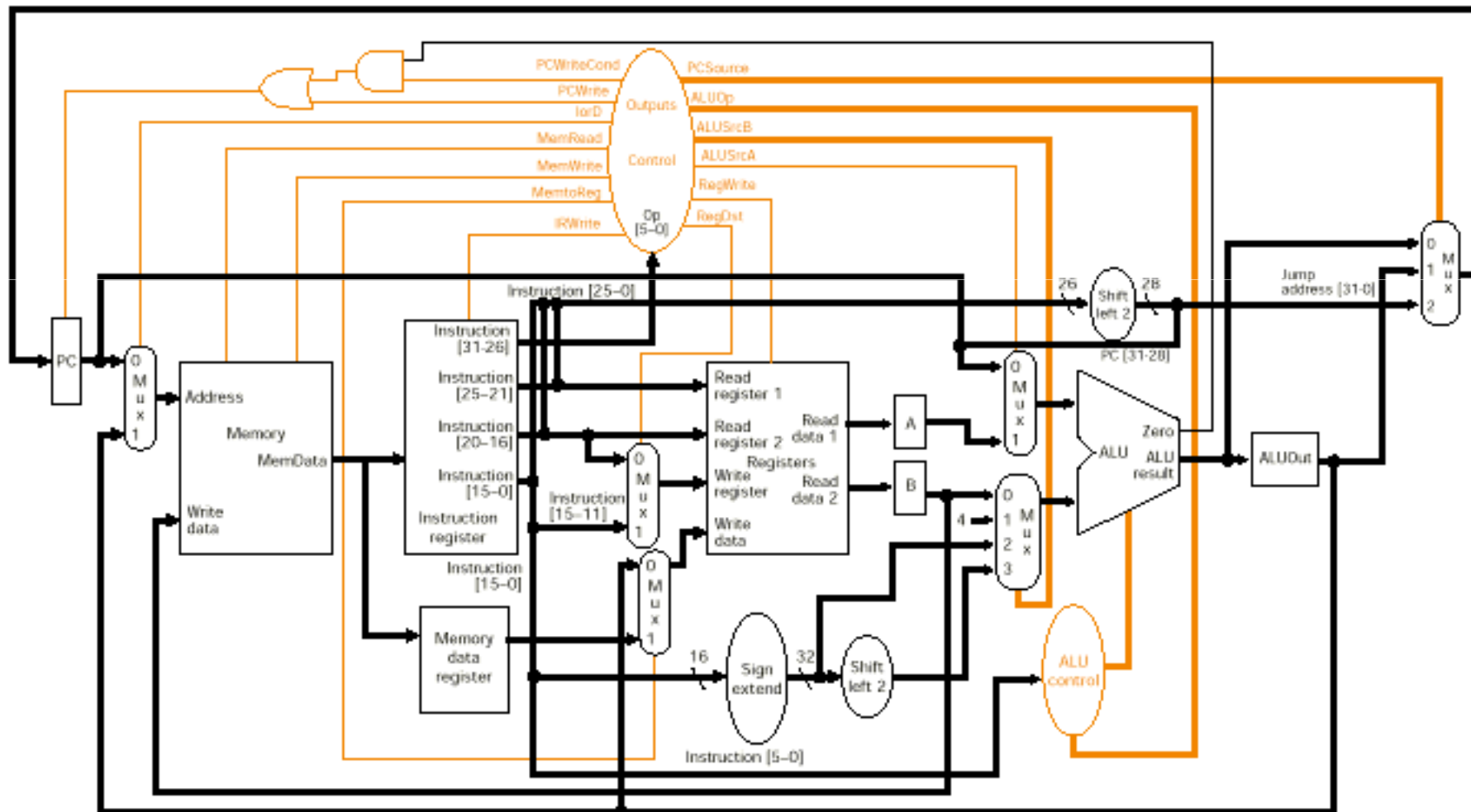

Recall MIPS Instruction Formats...

R-type Instructions



Load or Store



Branch



Jump




Execution Steps (1)

► Instruction Fetch

IR = Memory[PC];
PC = PC + 4;

Fetch

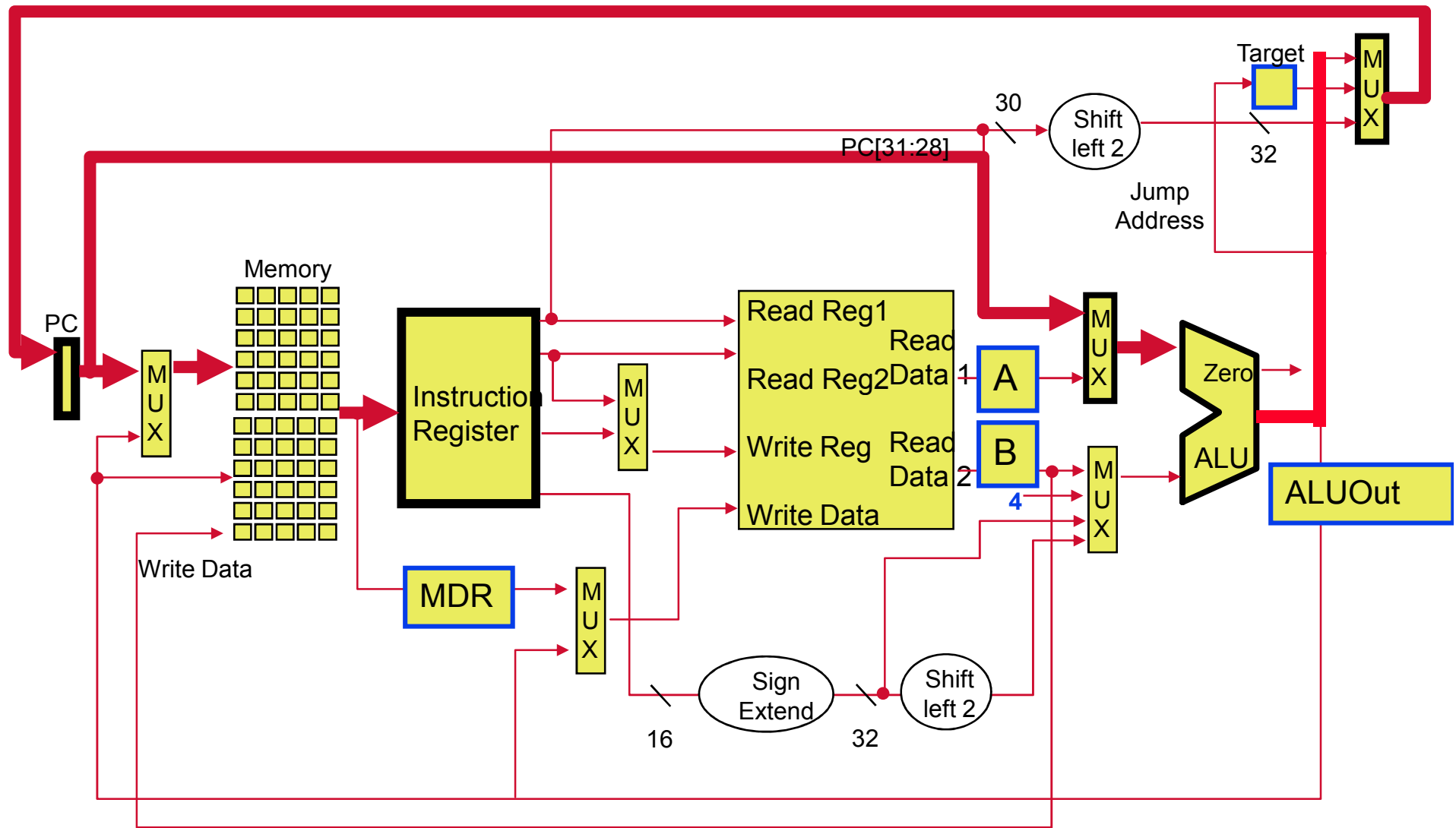

Execution Steps (2)


► Instruction Decode and Register Fetch

A = Reg[IR[25..21]];

B = Reg[IR[20..16]];

Target = PC + 4 + (signExtend(IR[15..0]) << 2);

Decode and Register Op Fetch

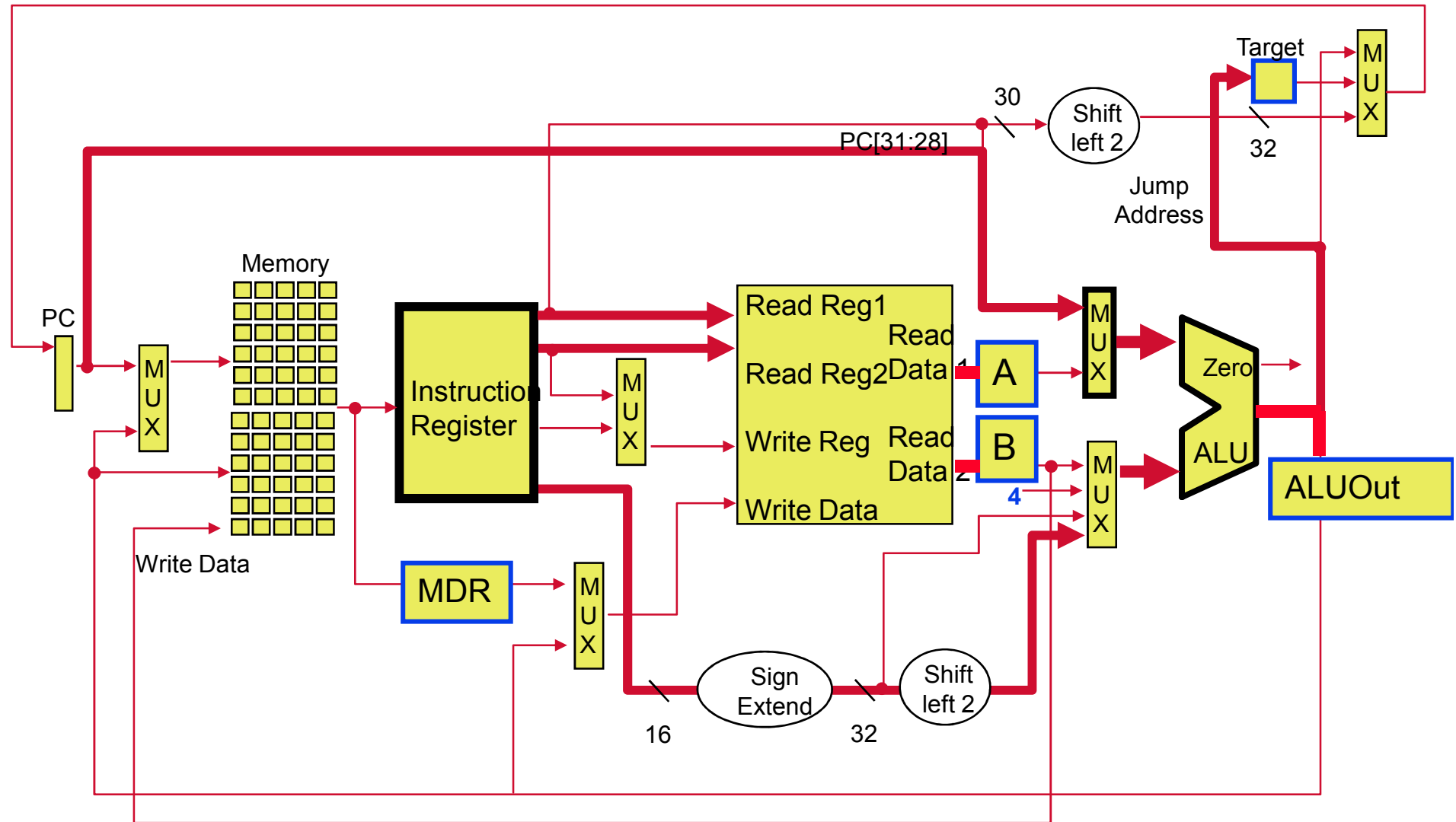

Execution Step (3)

► Execution, memory address computation or branch completion

▷ Memory Reference

$ALUOut = A + \text{signExtend}(IR[15..0]);$

▷ Arithmetic/Logical Operation

$ALUOut = A + B$


▷ Branch

If $(A == B)$ $PC = \text{Target};$

▷ Jump

$PC = PC[31 ..28] \parallel (IR[25..0] \ll 2);$

Execute (R-type)

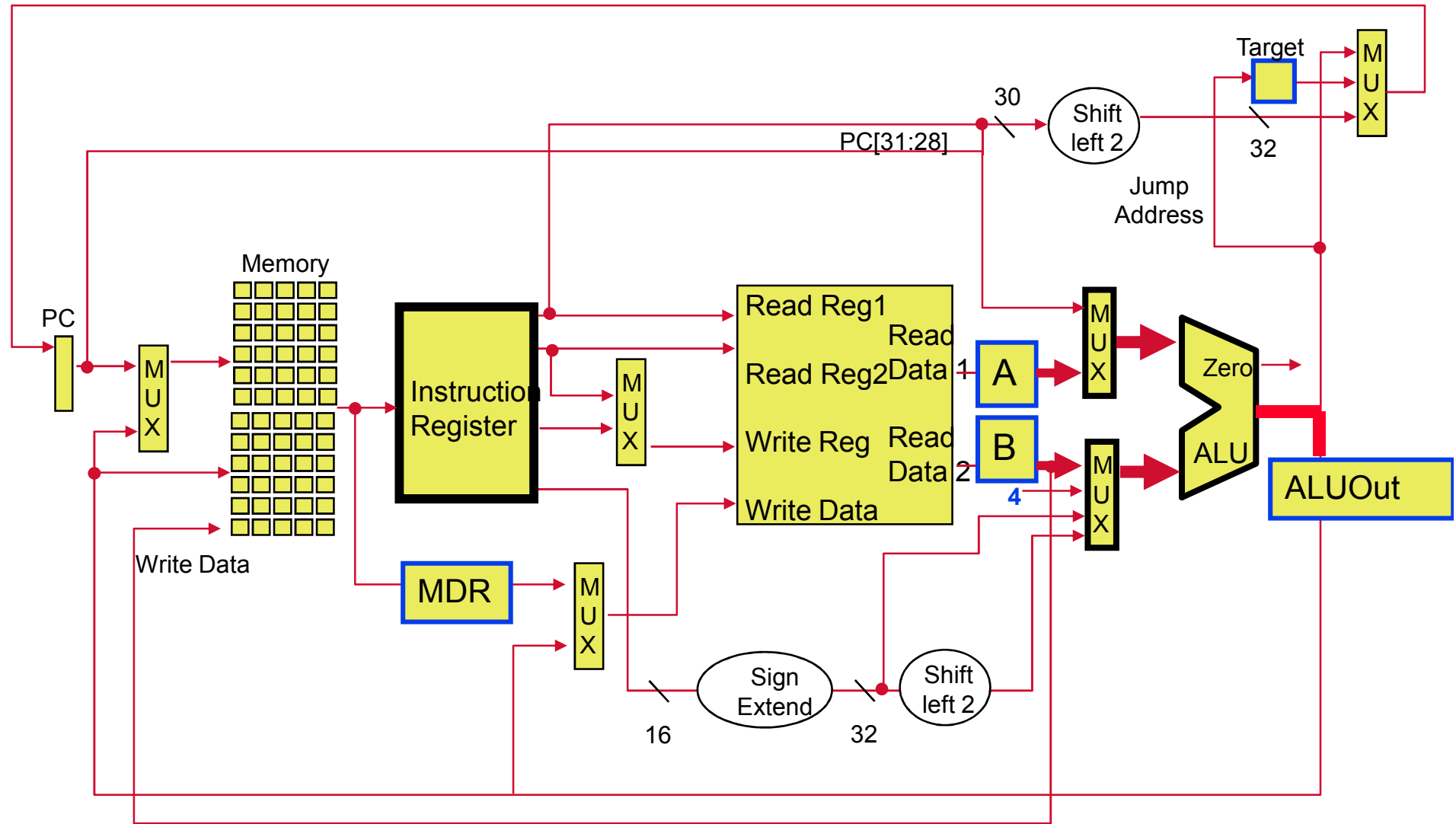

Execution Step (4)

► Memory access or R-type instruction completion

▷ Memory Reference

MDR = Memory[ALUOut];
or
Memory[ALUOut] = B;


▷ Arithmetic/Logical Instructions (R-type)

Reg[IR[15..11]] = ALUOut;

▷ Branch, Jump

Nothing

Execute (R-type)

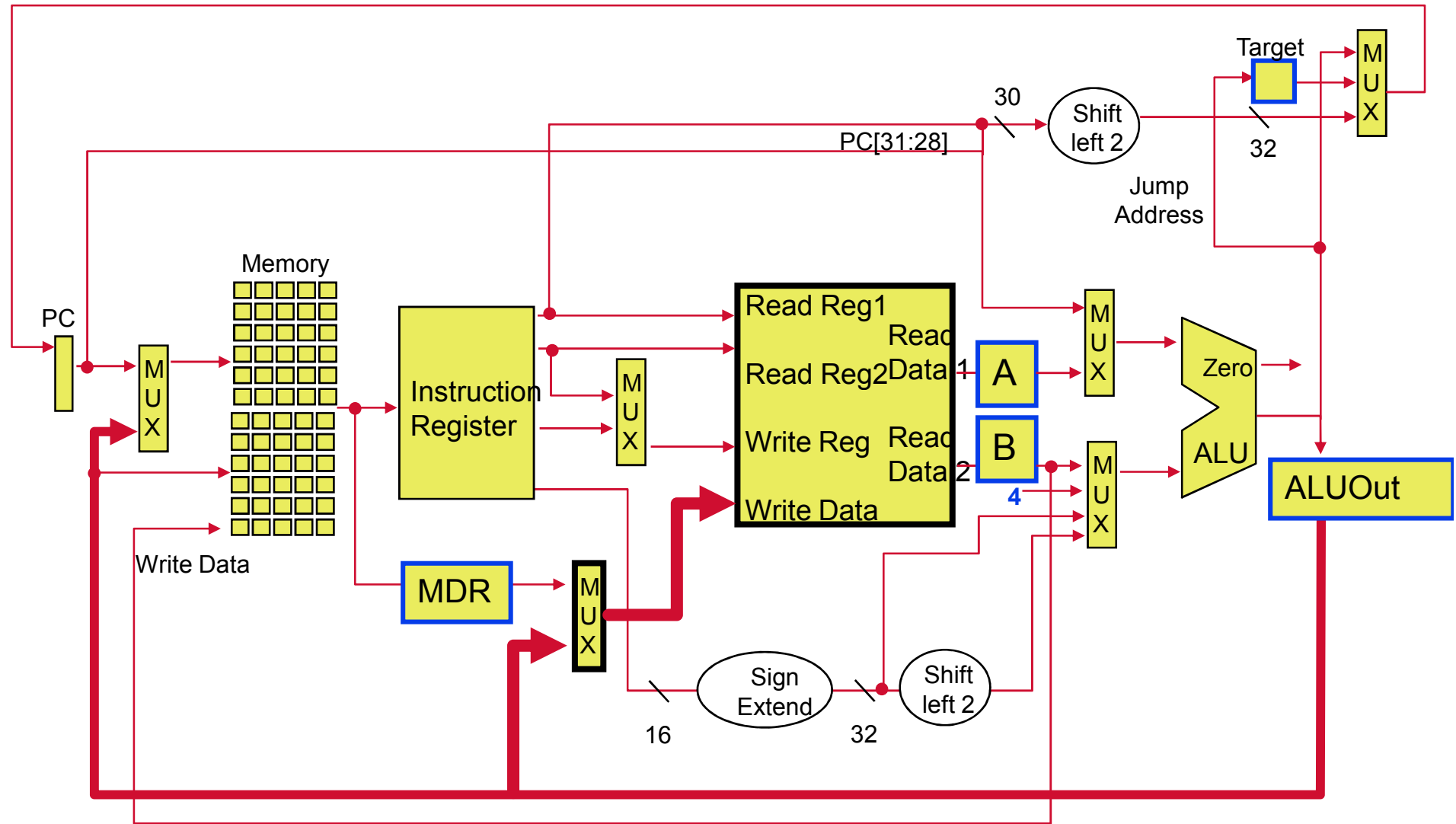


Execution Step (5)


- ▶ Memory Read completion (Load only)

Reg[IR[20..16]] = MDR;


Finite State Machine Control

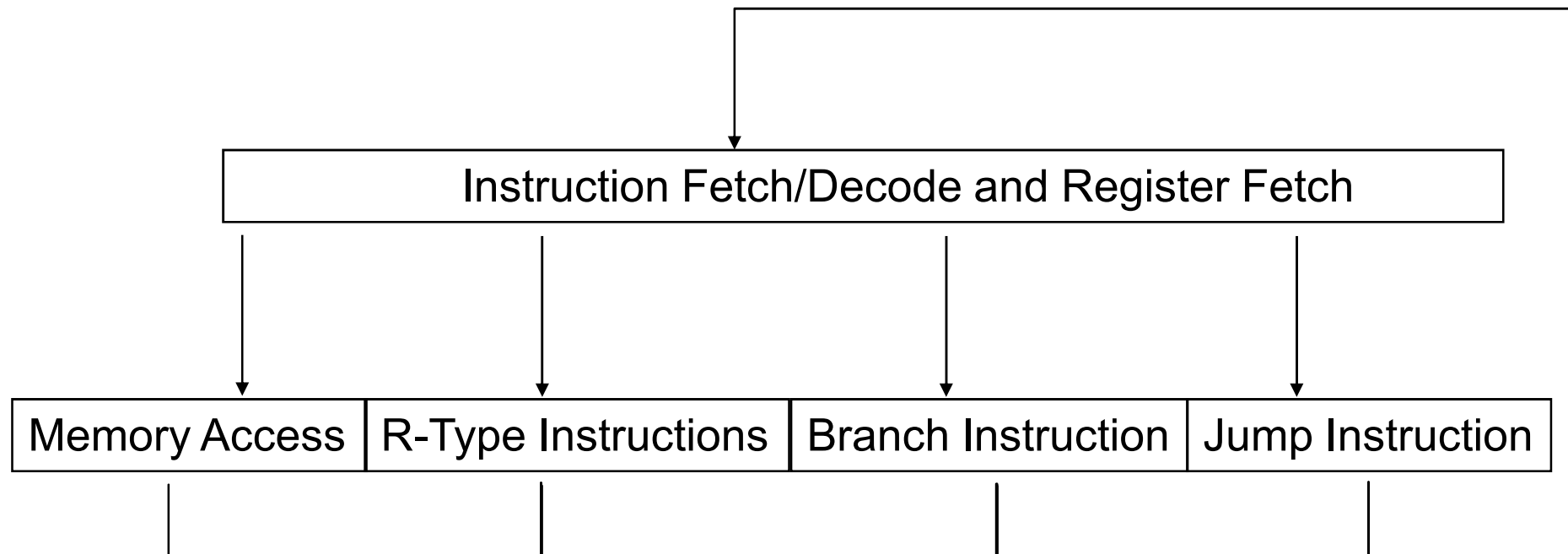


Multicycle Control

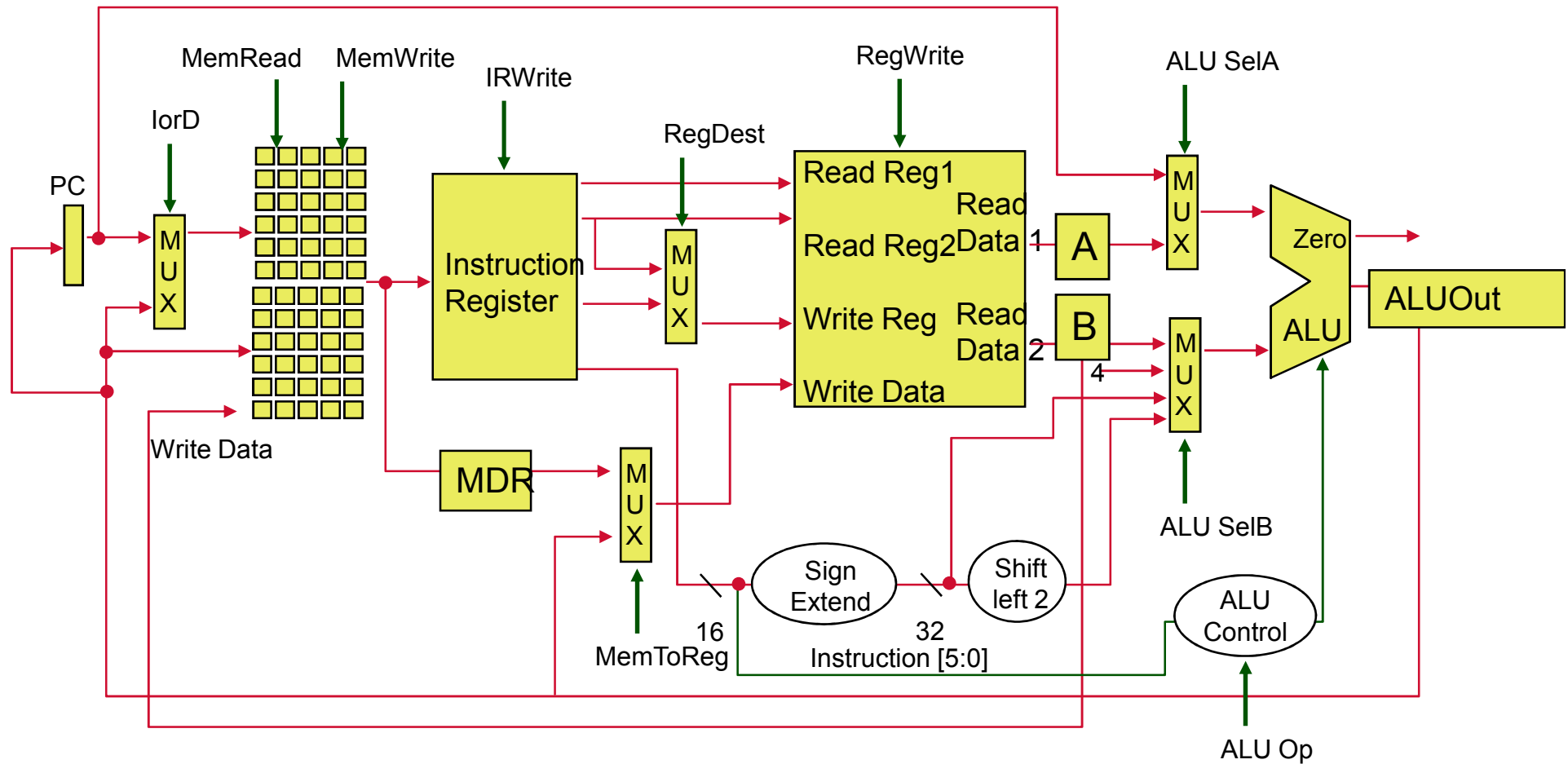


Instruction Fetch and Decode

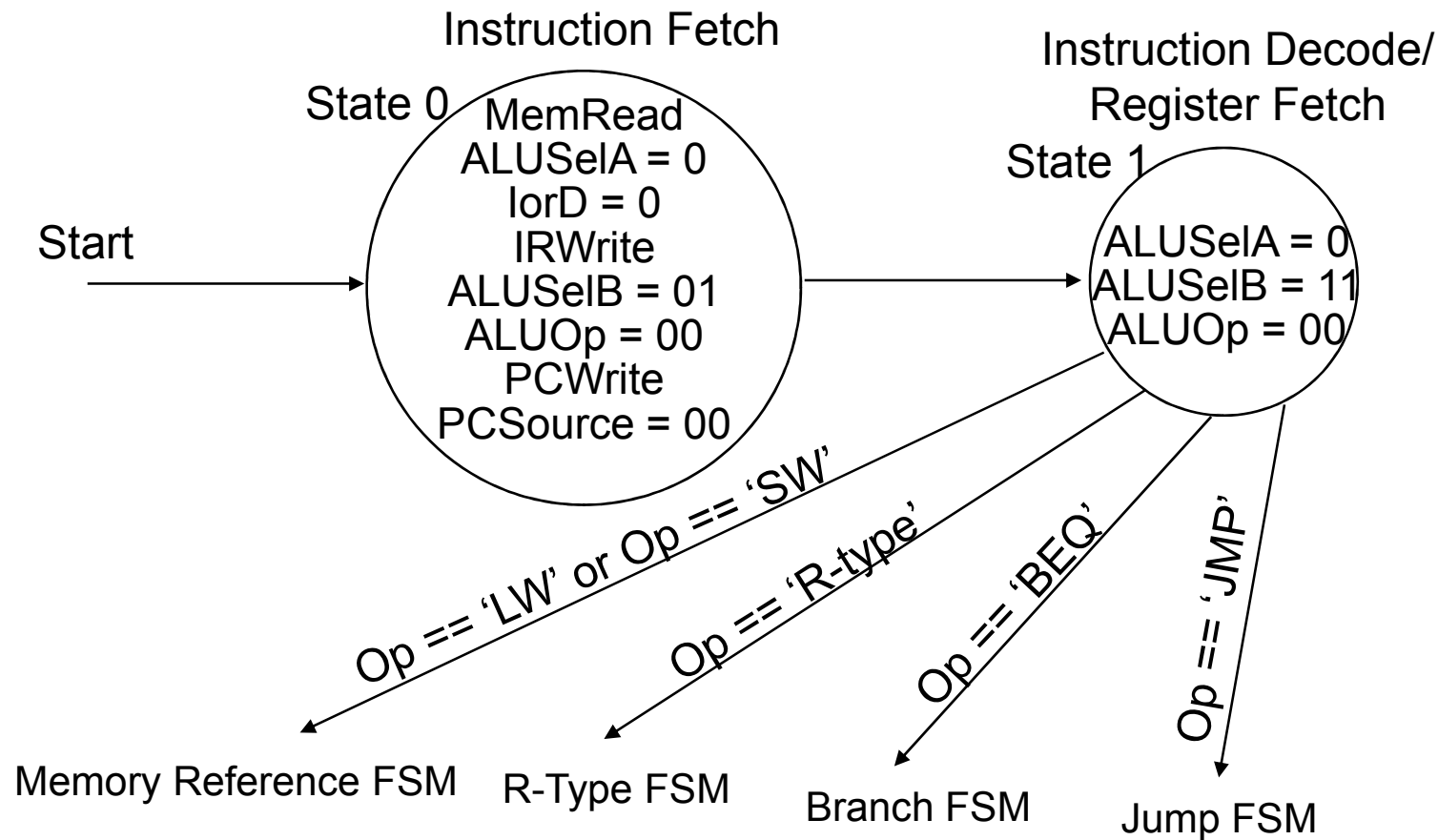


Memory-Reference FSM

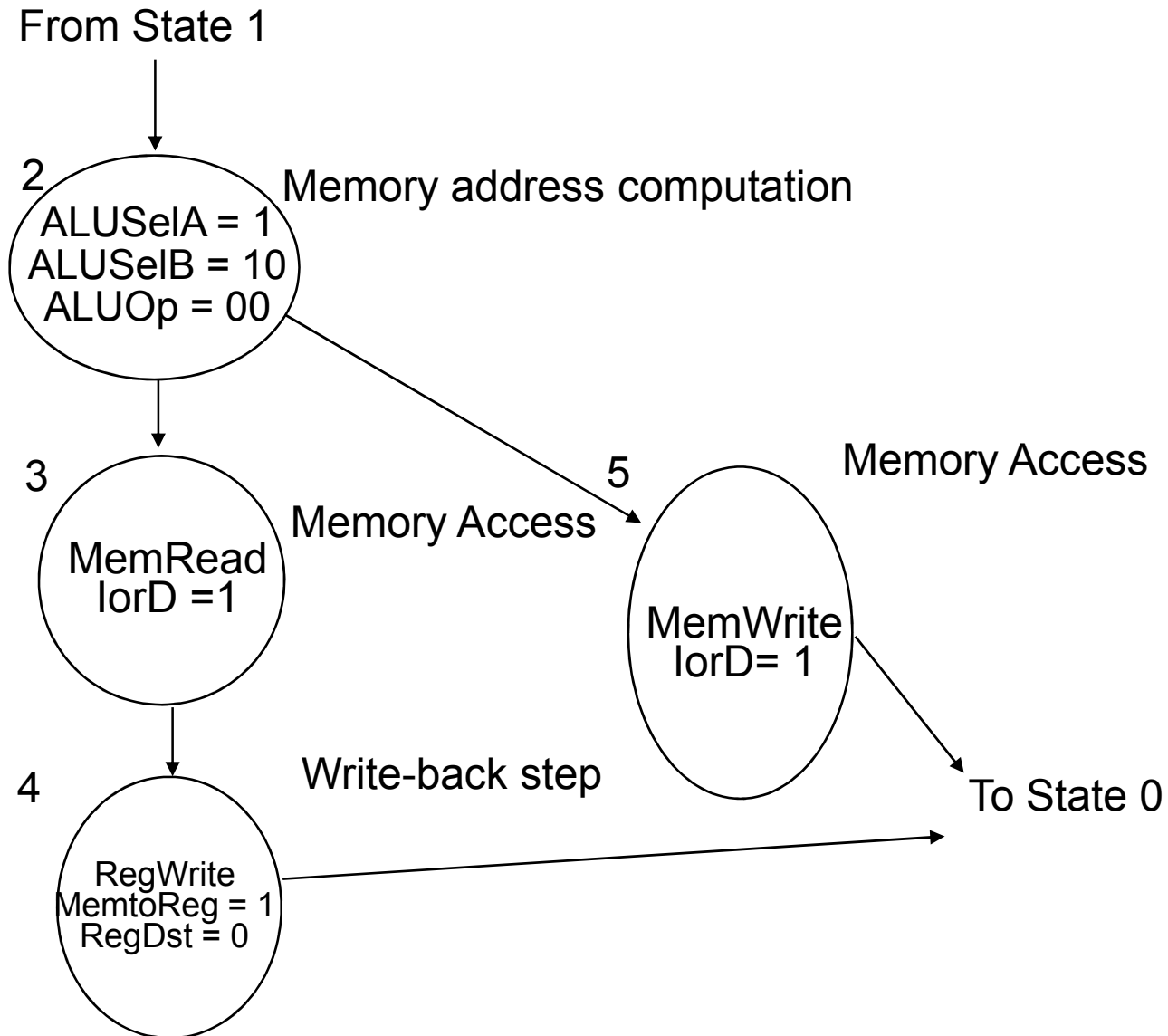


R-type FSM

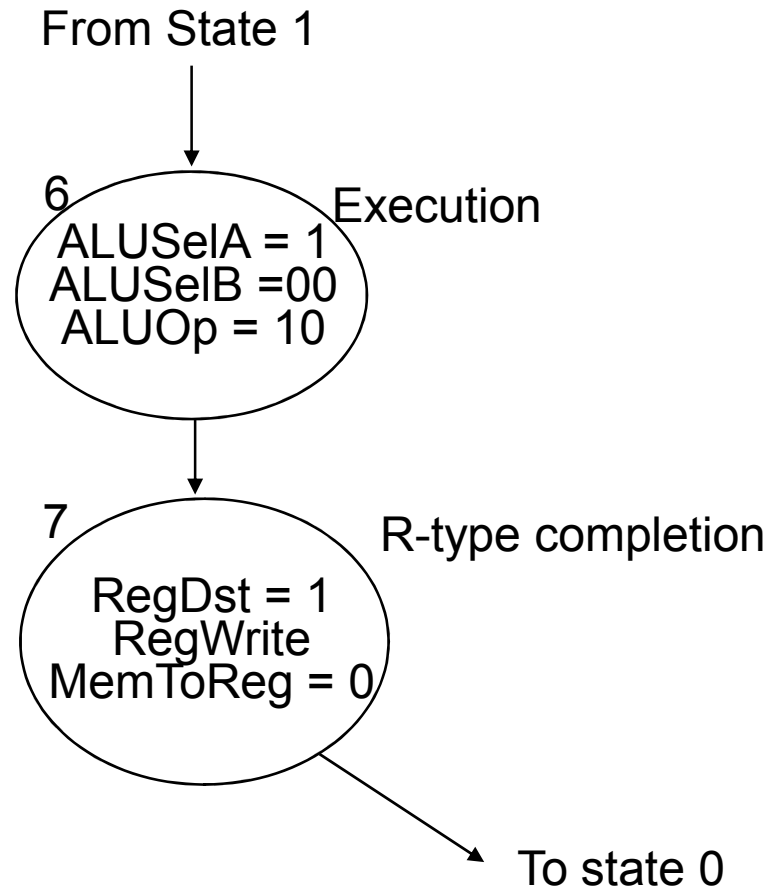

Branch FSM

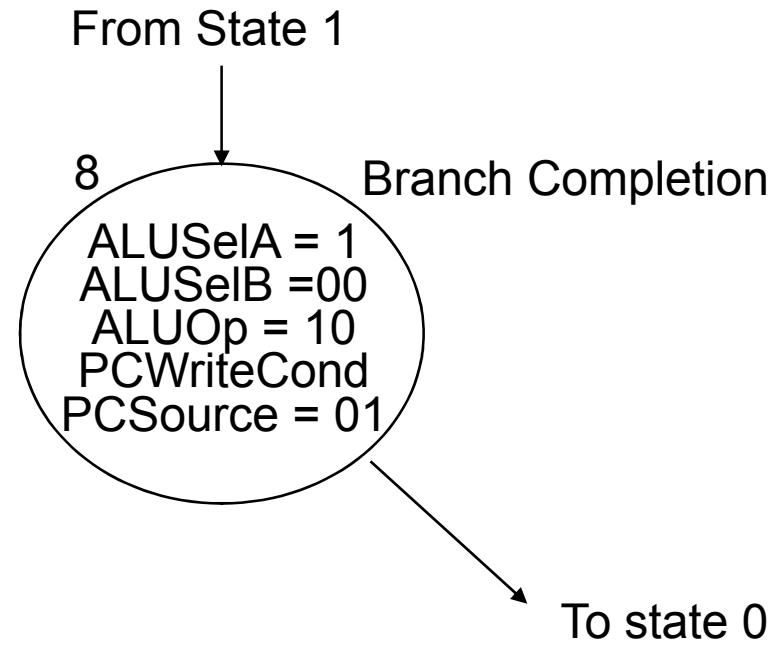


Jump FSM

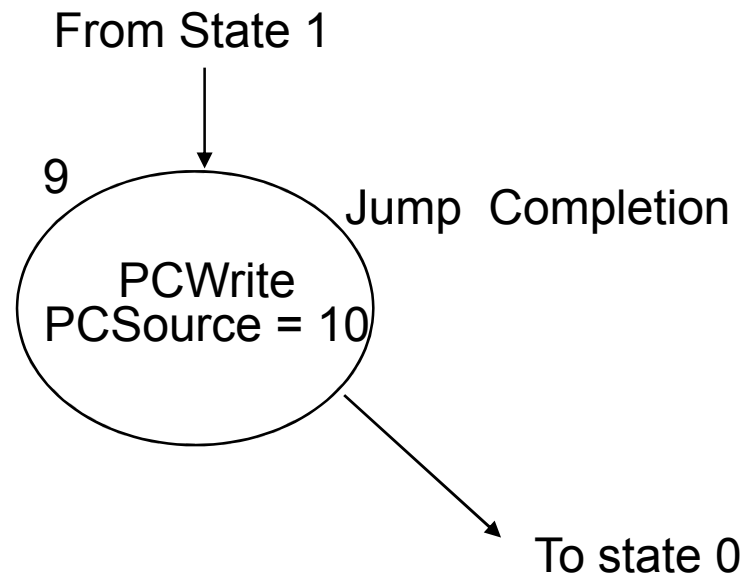


Complete State Diagram

► Figure 5.42 from book

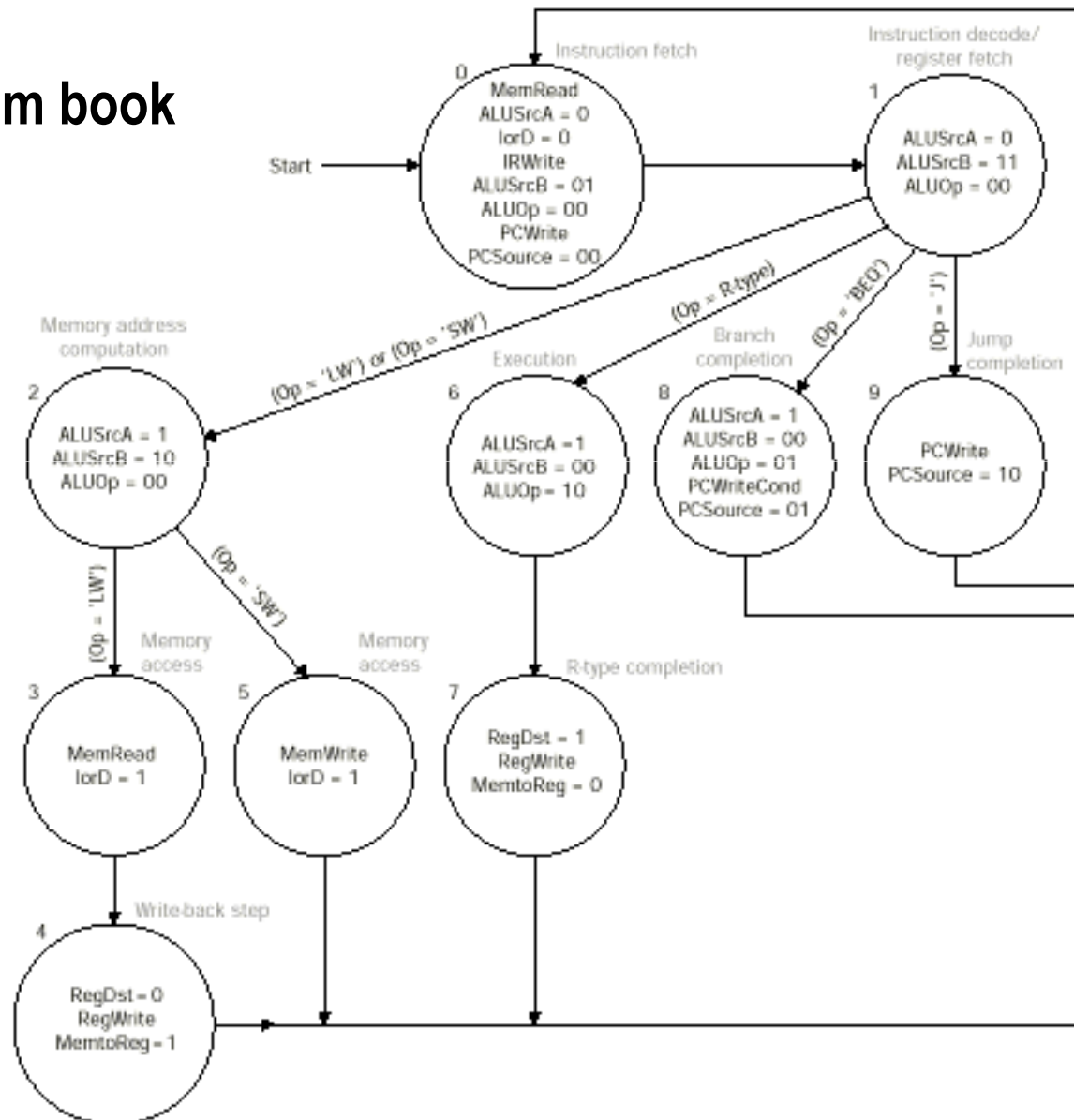

Multicycle Control

 

Performance of Multicycle Implementation

- ▶ Each type of instruction can take a variable # of cycles

- ▶ Example

- ▷ Assume the following instruction distributions:

▷ loads	5 cycles	22%
▷ stores	4 cycles	11%
▷ R-type	4 cycles	49%
▷ branches	3 cycles	16%
▷ jump	3 cycles	2%

- ▷ What's the average Cycles Per Instruction (CPI)

CPI = (CPU clock cycles/Instruction Count)

$$\text{CPI} = (5 \text{ cycles} * 0.22) + (4 \text{ cycles} * 0.11) + (4 \text{ cycles} * 0.49) \\ + (3 \text{ cycles} * 0.16) + (3 \text{ cycles} * 0.02)$$

CPI = 4.04 cycles per instruction

- ▷ What was the CPI for the single-cycle machine?

- ▷ Single cycle implies 1 clock cycle per instruction --> CPI = 1.0


- ▷ So isn't the single-cycle machine about 4 times faster?

Performance of Multicycle Implementation

- ▶ **The correct answer should consider the clock cycle time as well:**
 - ▷ For the single cycle implementation, the cycle time is given by the worst case delay: $T_{\text{cycle}} = 40\text{ns}$ (for load instructions, see slide 8)
 - ▷ For the multicycle implementation, the cycle time is given by the worst case delay over all execution steps: $T_{\text{cycle}} = 10\text{ ns}$ (for each of the steps 1, 2, 3, or 4).
- ▶ **The execution time per instruction is:**
 - ▷ $\text{CPI} * T_{\text{cycle}} = 40 * 1 = 40\text{ ns}$ per instruction for the single cycle machine
 - ▷ $\text{CPI} * T_{\text{cycle}} = 10 * 4.04 = 40.4\text{ ns}$ per instruction for the multicycle machine
 - ▷ Thus, the single cycle machine is **only 1% faster**
- ▶ **When considering other types of units (e.g., FP), the single cycle implementation can be very inefficient.**

Microcode: Another Approach

 - ▶ Another way to implement a Mealy machine:



N: Inputs

X: Outputs



S: State Bits

Storage:

$X + S$ (bits/word)

2^{N+S} (words)

Microcode II: Moore Machines

  

So who cares?

- ▶ **Imagine:**

- ▷ Hundreds of instructions...
- ▷ Tens of different instruction classes (we've seen four)
- ▷ Instructions that take anywhere from 1 to 100 cycles to complete


- ▷ That's what any real ISA has

- ▶ **Now imagine drawing the FSM diagram for that!**

- ▶ **Solution 1: Write Verilog and use synthesis (today)**


- ▶ **Solution 2: Use some programming lessons**

FSM structure

 

- ▶ **First cycles are the same**
- ▶ **No reconvergence after decode**
- ▶ **Limited Branching**

Exploiting the structure for microcode

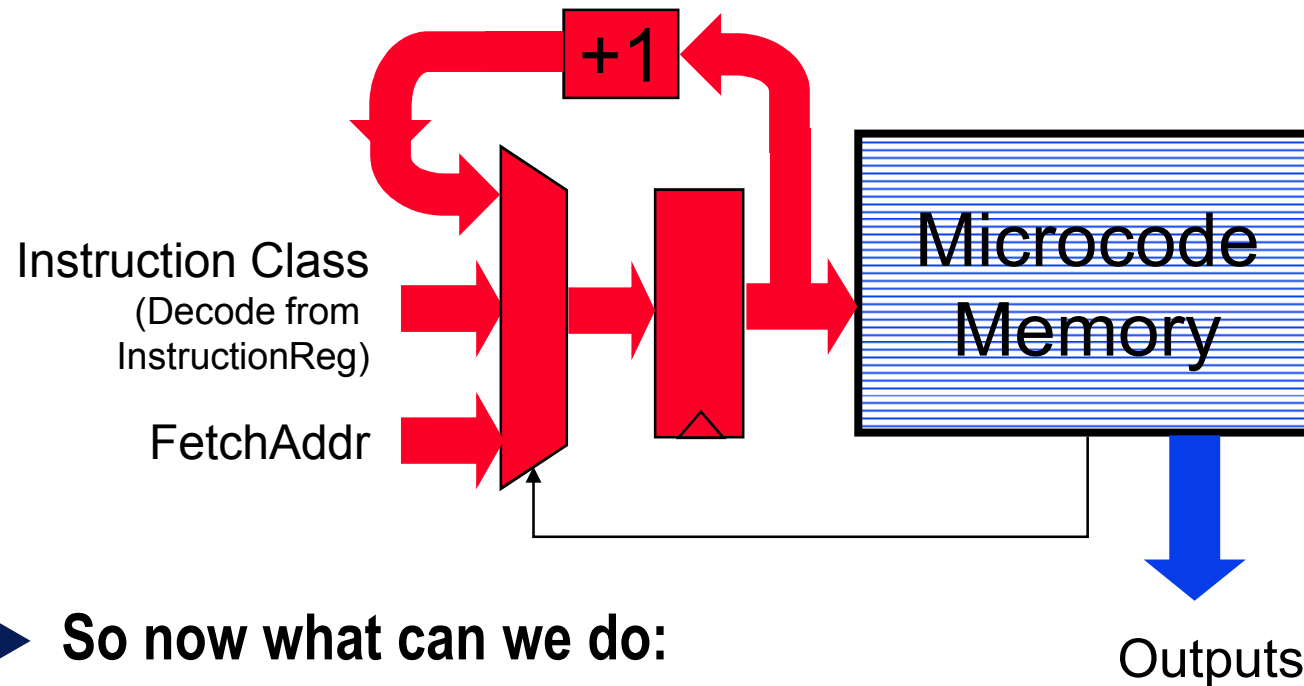

► So now what can we do:

- ▷ Go to instruction class address
- ▷ Go to the next word in the memory
- ▷ Go back to the fetch address

- ▷ Control everything by assigning bits in the word to control signals

Microcode Word Definition

- ▶ **ALU Control:** Add, Subt, Func code
- ▶ **SRC1:** PC, A
- ▶ **SRC2:** B, 4, Extend, Extshift
- ▶ **Register Control:** Read, Write ALU, Write MDR
- ▶ **Memory:** Read PC, Read ALU, Write ALU
- ▶ **PCWrite control:** ALU, ALUOut-cond, JumpAddress
- ▶ **Sequencing:** Seq, Fetch, Dispatch

- ▶ **Total Word Size ≥ 13**

Why is this nice?

- ▶ **Reduce complexity of control design**
 - ▷ Only way to do it before synthesis tools
 - ▷ Only way to encode Complex Instruction Sets
- ▶ **Allows bug fixes, optimizations after real hardware**
- ▶ **Now how do people do this today?**
- ▶ **Specify Style for:**
 - ▷ Registers
 - ▷ Latches
 - ▷ Combinational Logic
 - ▷ Finite State Machines

And Never Forget Marketing

- ▶ It is easy to sell a 1GHz processor
- ▶ It is harder to sell “Yes our processor is only 500MHz, but it actually achieves a lower CPI, and therefore really is higher performance.”

Other Multi-cycle Data Paths

- ▶ **Single cycle datapaths are strongly implied by ISA**
- ▶ **Is this true of multi-cycle implementations?**
 - ▷ NO!
 - ▷ There are a lot of possible data paths

Exceptions and Interrupts

- ▶ Exceptions are ‘**exceptional events**’ that disrupt the normal flow of a program
- ▶ Terminology varies between different machines
- ▶ Examples of **Interrupts**
 - ▷ User hitting the keyboard
 - ▷ Disk drive asking for attention
 - ▷ Arrival of a network packet
- ▶ Examples of **Exceptions**
 - ▷ Divide by zero
 - ▷ Overflow
 - ▷ Page fault


Handling Exceptions and Interrupts

- ▶ **When do we jump to an exception?**

- ▶ **Upon detection, invoke the OS to “service the event”**
 - ▷ Right when it occurs?
 - ▷ What about in the middle of executing a multi-cycle instruction
 - ▷ Difficult to abort the middle of an instruction
 - ▷ Processor checks for event at the end of every instruction
 - ▷ Processor provides EPC & Cause registers to inform OS of cause
 - ▷ **EPC** - Exception Program Counter
 - ▷ Holds PC that the OS should jump to when resuming execution
 - ▷ **Cause** Register
 - ▷ Holds bit-encoded cause of the exception

Exception Flow

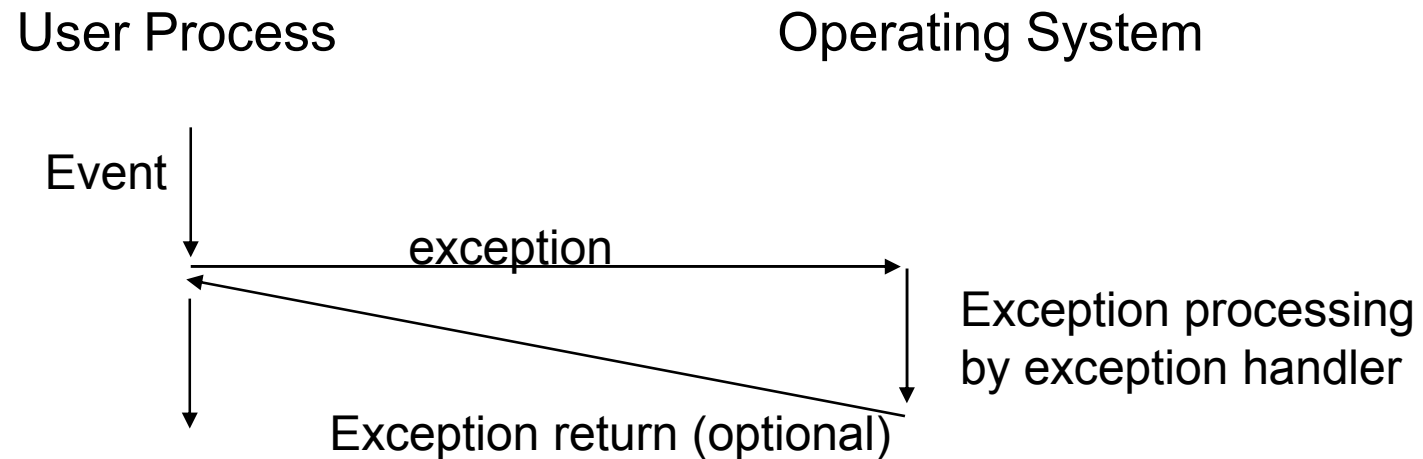- ▶ When an exception (or interrupt) occurs, control is transferred to the OS



Summary

- ▶ **Single cycle implementations have to consider the worst case delay through the datapath to come-up with the cycle time.**
- ▶ **Multicycle implementations have the advantage of using a different number of cycles for executing each instruction.**
- ▶ **In general, the multicycle machine is better than the single cycle machine, but the actual execution time strongly depends on the workload.**
- ▶ **The most widely used machine implementation is neither single cycle, nor multicycle – it's the pipelined implementation.**